

PRIPREMA ZA ISPIT ZNAKA - EL. STRUJNI KRUG, 2 dio

1. $Q = 30C$
 $W = 900J$

$U = ?$

$$U = \frac{W}{Q}$$

$$U = \frac{900J}{30C}$$

$$U = 30V$$

2. $U = 6V$
 $W = 3600J$

$Q = ?$

$$U = \frac{W}{Q}$$

$$Q = \frac{3600J}{6V}$$

$$Q = \frac{W}{U}$$

$$Q = 600C$$

3. $U = 220V$
 $Q = 3C$
 $W = ?$

$$U = \frac{W}{Q}$$

$$W = 220V \cdot 3C$$

$$W = U \cdot Q$$

$$W = 660J$$

4. $U = 4.5V$
 $I = 0.3A$
 $W = E = 0.0135kJ = 13.5J$

$t = ?$

$$W = U \cdot I \cdot t \quad | : UI$$

$$t = \frac{W}{UI}$$

$$t = \frac{13.5J}{4.5V \cdot 0.3A}$$

$$t = \frac{13.5J}{1.35VA} = 10s$$

$$t = 10s$$

5. a) $U = 9V$
 $U_1 = U_2 = U_3 = ?$

3 jednake žarulje
serijski spoj

$$U = U_1 + U_2 + U_3 = 3U_1$$

$$9V = 3U_1 \quad | :3$$

$$3V = U_1$$

$$U_1 = U_2 = U_3 = 3V$$

5b) $U = 4.5V + 4.5V = 9V$
serijski spoj izvora

$$U_1 = U_2 = U_3 = U = 9V$$

3 jednake žarulje,
paralelni spoj

5c) $U = 9V$
 $U_1 = U_2 = ?$
 $U_3 = ?$

$U = U_1 + U_2$ ista grana paralelnog spoja

$U_1 = U_2$ jednake žarulje spojene serijski

$$9V = U_1 + U_1$$

$$9V = 2U_1 \quad | :2$$

$$4.5V = U_1$$

$$U_1 = U_2 = 4.5V$$

$$U_3 = U = 9V$$



3. žarulja je u posebnoj
grani paralelnog spoja

6a) $U_{AB} = 12V$

b) $U_{AB} = \frac{U}{3} = \frac{12V}{3} = 4V$

c) $U_{AB} = 12V$

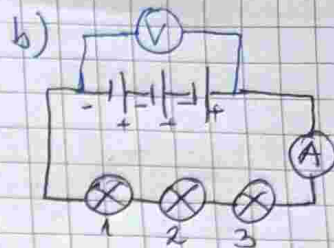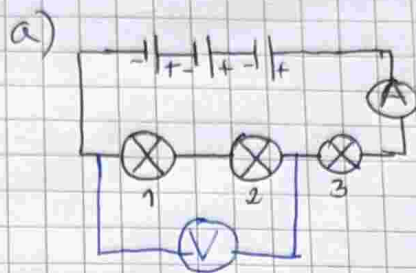7. a) napi napon na krajem ž (1) i (2)
b) napi napon izvora



8a) $U = 9V$

$U_1 = 3V$

$U_2 = ?$

$U = U_1 + U_2$

$U_2 = U - U_1$

$U_2 = 9V - 3V$

$U_2 = 6V$

b) $Q = 1C$

$U = 9V$

$\Delta E = ?$

$\Delta E = W$

$U = \frac{W}{Q}$

$W = U \cdot Q$

$W = 9V \cdot 1C$

$W = 9J$

c) $U_A = 3V$

$Q = 1C$

$W = ?$

$W = \Delta E$

$W = U_A \cdot Q$

$W = 3V \cdot 1C$

$W = 3J$

9.

$I = 60A$

$U = 230V$

$P = ?$

$P = UI$

$P = 230V \cdot 60A$

$P = 13800W$

10. $t = 8h$

$U = 220V$

$I = 5.5A$

$\Delta E = ?$

$\Delta E = W$

$W = UI t$

$W = 220V \cdot 5.5A \cdot 8h$

$W = 1210W \cdot 8h$

$W = 9680Wh$

$W = 9.68kWh$

ili

$W = 220V \cdot 5.5A \cdot 28800s$

$W = 34848000J$

11. $P = 1.4kW$

$t = 1h$

$W = ?$

$P = \frac{W}{t}$

$W = P \cdot t$

$W = 1.4kW \cdot 1h$

$W = 1.4kWh$

12. $P = 1.2kW = 1200W$

$U = 220V$

a) $I = ?$

$P = UI$

$I = \frac{P}{U}$

$I = 1200W : 220V$

$I = 5.45A$

b) $t = 4h$
 $W = ?$

$W = UI t$

$W = 220V \cdot 5.5A \cdot 4h$

$W = 4796Wh = 4.796kWh$

$$13. \quad I = 2.5 \text{ A}$$

$$P = 275 \text{ W}$$

$$U = ?$$

$$P = UI$$

$$275 \text{ W} = U \cdot 2.5 \text{ A} \quad | : 2.5 \text{ A}$$

$$U = \frac{275 \text{ W}}{2.5 \text{ A}}$$

$$\boxed{U = 110 \text{ V}}$$

$$16. \quad t = 14 \text{ d} \cdot 24 \text{ h} = 336 \text{ h}$$

$$P = 100 \text{ W}$$

$$\text{cena } 0.4 \text{ kn/kWh}$$

odkum?

$$P = \frac{W}{t}$$

$$W = P \cdot t$$

$$W = 100 \text{ W} \cdot 336 \text{ h}$$

$$W = 33600 \text{ Wh}$$

$$W = 33.6 \text{ kWh}$$

$$\text{množka (cena)} = 33.6 \text{ kWh} \cdot 0.4 \text{ kn/kWh}$$

$$= \boxed{13.44 \text{ kn}}$$

Platit ćemo 13.44 kune.

$$19. \quad R = 40 \Omega$$

$$I = 25 \text{ mA} = 0.025 \text{ A}$$

$$U = ?$$

$$I = \frac{U}{R}$$

$$U = I \cdot R$$

$$U = 0.025 \text{ A} \cdot 40 \Omega$$

$$\boxed{U = 1 \text{ V}}$$

$$14. \quad P = 500 \text{ W}$$

$$W = 6 \text{ kJ} = 6000 \text{ J}$$

$$t = ?$$

$$P = \frac{W}{t}$$

$$t = \frac{W}{P}$$

$$t = \frac{6000 \text{ J}}{500 \text{ W}}$$

$$\boxed{t = 12 \text{ s}}$$

$$15. \quad U = 220 \text{ V}$$

$$t = 1 \text{ h}$$

$$Q = 900 \text{ C}$$

$$P = ?$$

$$I = \frac{Q}{t}$$

$$I = \frac{900 \text{ C}}{3600 \text{ s}}$$

$$I = 0.25 \text{ A}$$

$$P = UI$$

$$P = 220 \text{ V} \cdot 0.25 \text{ A}$$

$$\boxed{P = 55 \text{ W}}$$

$$17. \quad R = 2 \text{ k}\Omega = 2000 \Omega$$

$$U = 220 \text{ V}$$

$$I = ?$$

$$I = \frac{U}{R}$$

$$\boxed{I = \frac{220 \text{ V}}{2000 \Omega} = 0.11 \text{ A}}$$

$$\boxed{I = 0.11 \text{ A}}$$

$$18. \quad R = 50 \Omega$$

$$I = 0.2 \text{ A}$$

$$U = ?$$

$$I = \frac{U}{R}$$

$$U = I \cdot R$$

$$U = 0.2 \text{ A} \cdot 50 \Omega$$

$$\boxed{U = 10 \text{ V}}$$

$$21. \quad R = 3 \Omega$$

$$t = 2 \text{ min} = 120 \text{ s}$$

$$U = 4.5 \text{ V}$$

$$Q = ?$$

$$I = \frac{U}{R}$$

$$I = \frac{4.5 \text{ V}}{3 \Omega}$$

$$\underline{I = 1.5 \text{ A}}$$

$$I = \frac{Q}{t}$$

$$Q = I \cdot t$$

$$Q = 1.5 \text{ A} \cdot 120 \text{ s}$$

$$\boxed{Q = 180 \text{ C}}$$

$$20. \quad U = 220 \text{ V}$$

$$I = 2 \text{ A}$$

$$R = ?$$

$$I = \frac{U}{R}$$

$$R = \frac{U}{I}$$

$$R = \frac{220 \text{ V}}{2 \text{ A}}$$

$$R = 110 \Omega$$

22. $U = 220V$
 $t = 3 \text{ min} = 180s$
 $Q = 3600C$
 $R = ?$

$$I = \frac{Q}{t}$$

$$I = \frac{3600C}{180s}$$


$$I = 20A$$

$$R = \frac{U}{I}$$

$$R = \frac{220V}{20A}$$

$$R = 11\Omega$$

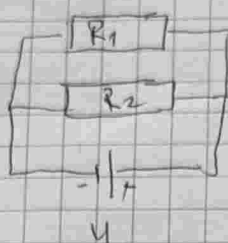23. $R_1 = 2\Omega$
 $R_2 = 8\Omega$
 po nelinearni spoj
 $R = ?$



$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{2\Omega} + \frac{1}{8\Omega}$$

$$\frac{1}{R} = \frac{4+1}{8\Omega} = \frac{5}{8\Omega}$$

$$R = \frac{8\Omega}{5} = 1.6\Omega$$

24. $R_1 = 7\Omega$
 $R_2 = 5\Omega$
 serijski spoj

$$R = R_1 + R_2$$

$$R = 7\Omega + 5\Omega$$

$$R = 12\Omega$$

25. a) $R_{uc} = R = 2\Omega$

b) $R_{uc} = 2R = 4\Omega$

c) $\frac{1}{R_{uc}} = \frac{1}{R} + \frac{1}{R}$

$$\frac{1}{R_{uc}} = \frac{2}{R}$$

$$R_{uc} = \frac{R}{2} = 1\Omega$$

u c) najveci
 struja je
 otpor najmanji;
 a u b) najmanja
 je otpor najveći.

veći otpor → manja struja.

26. $R_1 = 4\Omega$

a) $R_2 = 2\Omega$

$R_3 = 2\Omega$

$R = ?$

$$\frac{1}{R_{1,3}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{2,3}} = \frac{1}{2\Omega} + \frac{1}{2\Omega} = \frac{2}{2\Omega}$$

$$R_{2,3} = \frac{2\Omega}{2} = 1\Omega$$

$$R = R_1 + R_{2,3}$$

$$R = 4\Omega + 1\Omega = 5\Omega$$

26. b) $R_1 = 4\Omega$
 $R_2 = 4\Omega$
 $R_3 = 2\Omega$
 $R = ?$

$$R_{1,2} = R_1 + R_2$$

$$R_{1,2} = 4\Omega + 4\Omega$$

$$R_{1,2} = 8\Omega$$

$$\frac{1}{R} = \frac{1}{R_{1,2}} + \frac{1}{R_3}$$

$$\frac{1}{R} = \frac{1}{8\Omega} + \frac{1}{2\Omega}$$

$$\frac{1}{R} = \frac{1+4}{8\Omega} = \frac{5}{8\Omega}$$

$$R = \frac{8\Omega}{5} = 1.6\Omega$$

27.

a) $I = 2A$

b) $I = 2A, U = 8V$
 $R = ?$

$$R = \frac{U}{I}$$

$$R = \frac{8V}{2A} = 4\Omega$$

c) $R = 4\Omega$
 $U = 16V$
 $I = ?$


$$I = \frac{U}{R}$$

$$I = \frac{16V}{4\Omega}$$

$$I = 4A$$


li napon 2x veci,
 struja 2x veci.

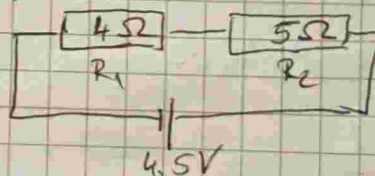28. $R_1 = 4\Omega, R_2 = 5\Omega$ skema?
 $U = 4.5V$



29. $R_1 = 25 \Omega$
 $R_2 = 100 \Omega$
 $U = 220V$
paralelný spoj

$I = ?$

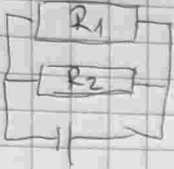

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \frac{1}{25 \Omega} + \frac{1}{100 \Omega}$$

$$\frac{1}{R} = \frac{4+1}{100 \Omega} = \frac{5}{100 \Omega}$$


$$R = \frac{100 \Omega}{5} = 20 \Omega$$

$$I = \frac{U}{R}$$

$$I = \frac{220V}{20 \Omega}$$

$$I = 11A$$

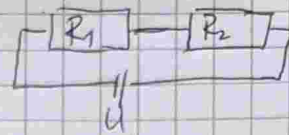30. $R_1 = 6 \Omega$
 $R_2 = 4 \Omega$
 $U = 20V$



a) $R = ?$

$$R = R_1 + R_2$$

$$R = 6 \Omega + 4 \Omega$$

$$R = 10 \Omega$$

c) $U_1 = ?$
 $U_2 = ?$

$$I_1 = \frac{U_1}{R_1}$$

$$U_1 = I_1 R_1$$

$$I = I_1 = 2A$$

$$U_1 = 2A \cdot 6 \Omega$$

$$U_1 = 12V$$

b) $I = \frac{U}{R}$

$$I = \frac{20V}{10 \Omega}$$

$$I = 2A$$

$$I = I_2 = 2A$$

$$U_2 = I_2 R_2$$

$$U_2 = 2A \cdot 4 \Omega$$

$$U_2 = 8V$$

31. $t = 2s$
 $Q = 4C$
 $I = ?$

$$I = \frac{Q}{t}$$

$$I = \frac{4C}{2s}$$

$$I = 2A$$

32. $Q = 1C$
 $I = 0.04A$
 $t = ?$

$$I = \frac{Q}{t}$$

$$t = \frac{Q}{I}$$

$$t = \frac{1C}{0.04A}$$

$$t = 25s$$

33. $t = 1min = 60s$
 $I = 0.6A$
 $Q = ?$

$$Q = I \cdot t$$

$$Q = 0.6A \cdot 60s$$

$$Q = 36C$$

34. $t = 2min$
 $Q_1 = 4800C$
 $Q_2 = 80C$

První vodičem
 teče jádra smyslu
 je bu kolektoru
 impetu vodičem
 protače uca kolicina
 mabaja.

35. $t = 1h = 3600s$
 $I = 5A$

$$Q = ?$$

$$Q = I t$$

$$Q = 5A \cdot 3600s$$

$$Q = 18000C$$

Zadatok 1

a) $I = 0.3A$

b) $I_2 = 0.5A - 0.2A$
 $I_2 = 0.3A$

c) $I = I_1 + I_2$
 $I = 0.1A + 0.3A$
 $I = 0.4A$

d) $I_2 = I_3 = I_1 = 0.3A$

Zadatok 2

$I_1 = 0.5A$
 $t = 1min = 60s$

Q u kanyfi 2

$$Q = I_2 \cdot t$$

$$I_2 = I_1 = 0.25A$$

$$Q = 0.25A \cdot 60s$$

$$Q = 15A$$

ZADATOK 3

